

3. Current Electricity

Question 1:

The accompanying figure shows some electrical appliances connected in a circuit in a house. Answer the following questions.




1. By which method are the appliances connected?
2. What must be the potential difference across individual appliances?
3. Will the current passing through each appliance be the same? Justify your answer.
4. Why are the domestic appliances connected in this way?
5. If the T.V. stops working, will the other appliances also stop working? Explain your answer.

Answer

1. The appliances are in parallel connection.
2. The potential difference across each appliance should be same as they are connected in parallel.
3. No, the current passing through each appliance is not same. From Ohm's law, the current flowing through each appliance is $I=V/R$. Since, potential difference across each appliance is same, each appliance can have different resistance and $I \propto 1/R$, therefore, the current flowing through them will be different.
4. Domestic appliance are connected in parallel because, even if one or more appliances get faulty or stops working, the working of others will remain unaffected.
5. As the appliances are connected parallel across the supply. The working of other appliances will remain unaffected even if the T.V. stops working.

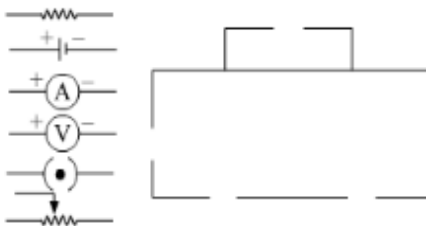Question 2:


The following figure shows the symbols for components used in the accompanying electrical circuit. Place them at proper places and complete the circuit.



Which law can you prove with the help of the above circuit?

Answer

Ohm's law $I=V/R$ can be proved with the help of above circuit.

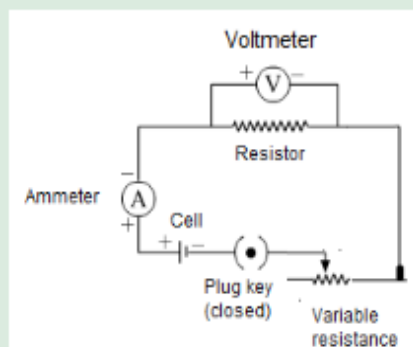

Question 3:

Umesh has two bulbs having resistances of $15\ \Omega$ and $30\ \Omega$. He wants to connect them in a circuit, but if he connects them one at a time the filament gets burnt.

Answer the following.

- Which method should he use to connect the bulbs?
- What are the characteristics of this way of connecting the bulbs depending on the answer of A above?
- What will be the effective resistance in the above circuit?

Answer

A. If bulbs are connected in series, the effective resistance of the circuit increases and hence current through the bulbs decreases. In this way, both the bulbs can be saved from burning.

B. Following are the characteristics of series connection:

- The effective resistance of the circuit is the sum of individual resistance of the resistors present in the circuit.
- The effective resistance of the series circuit is always larger than the greatest resistance in the circuit.
- Current through various electrical components connected in series is same.
- The source voltage gets divided across the electrical components connected in series.

C. The effective resistance of the circuit = $15\ \Omega + 30\ \Omega = 45\ \Omega$

Question 4:

The following table shows current in Amperes and potential difference in Volts.

V (Volts)	I (Amp)
4	9
5	11.25
6	13.5

- Find the average resistance.
- What will be the nature of the graph between the current and potential difference? (Do not draw a graph.)
- Which law will the graph prove? Explain the law.

Answer

(i). From Ohm's law, we have

$$R = V/I$$

V (volts)	I (amp)	R (ohm)
4	9	$4/9=0.44$
5	11.25	$5/11.25=0.44$
6	13.5	$6/13.5=0.44$

Therefore, average resistance = $(0.44+0.44+0.44)/3 = 0.44\ \Omega$

(ii) The nature of the graph between the current and potential difference will be a straight line passing through origin (0,0).

(iii) The graph proves Ohm's law. Ohm's law states that, under constant temperature and physical conditions, the current flowing through a conductor is always proportional to the potential difference across it i.e. $V \propto I$ or, $V = RI$

Question 5:

Match the pairs

'A' Group	'B' Group
1. Free electrons	a. V/R
2. Current	b. Increases the resistance in the circuit
3. Resistivity	c. Weakly attached
4. Resistances in series	d. VA/LI

Answer

'A' Group	'B' Group
1. Free electrons	c. Weakly attached
2. Current	a. V/R
3. Resistivity	d. VA/LI
4. Resistances in series	b. Increases the resistance in the circuit

Question 6:

The resistance of a conductor of length x is r . If its area of cross-section is a , what is its resistivity? What is its unit?

Answer

We know $R = \rho(L/A)$

\therefore Resistivity of a conductor, $\rho = RA / L$


Here, $L = x$, $R = r$ and $A = a$

Therefore, $\rho = ra / x$

The unit of resistivity is ohm-metre ($\Omega\text{-m}$).

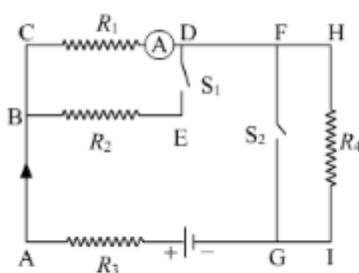Question 7:


Resistances R_1 , R_2 , R_3 and R_4 are connected as shown in the figure. S_1 and S_2 are two keys. Discuss the current flowing in the circuit in the following cases.



(i) Both S_1 and S_2 are closed.

Answer

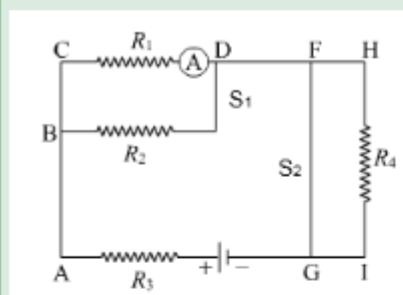(i) The circuit for this case is shown below.



R_4 is shunted by S_2 . Hence the Resistance of this combination will be practically zero

R_1 and R_2 in parallel

$$\therefore \frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\therefore R_p = \frac{R_1 R_2}{R_1 + R_2}$$

R_3 and R_p in series

$$\therefore R_s = R_3 + R_p$$

$$\therefore I_3 = \frac{V}{R_s} = \frac{V}{R_3 + R_p}$$

$$V_1 = V - I_3 R_3$$

$$= V - \frac{R_3 V}{R_3 + R_p}$$

$$= V \left(1 - \frac{R_3}{R_3 + R_p} \right)$$

$$= V \left(\frac{R_p}{R_3 + R_p} \right)$$

$$\therefore I_1 = V_1 / R_1 = \frac{V}{R_1} \left(\frac{R_p}{R_3 + R_p} \right)$$


Similarly

$$I_2 = \frac{V}{R_2} \left(\frac{R_p}{R_3 + R_p} \right)$$

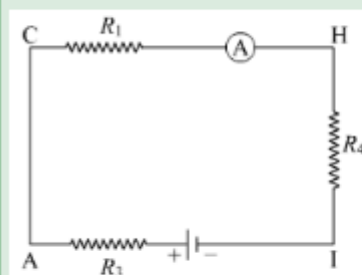(ii) Both S_1 and S_2 are open.

Answer

The circuit for this case is shown below.



Here, R_1 , R_4 and R_3 are in series. Therefore, the equivalent resistance of the circuit is

$$R_{eq} = R_1 + R_3 + R_4$$

Hence, the current flowing in the circuit is


$$I = \frac{V}{R_{eq}} = \frac{V}{R_1 + R_3 + R_4}$$

where, V is the potential difference of the battery.

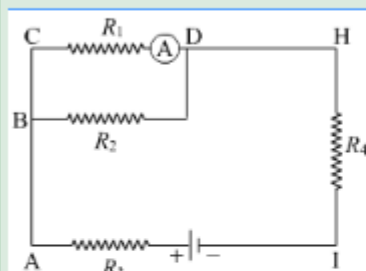(iii) S_1 is closed but S_2 is open.


Answer

The circuit for this case is shown below.



Here, R_1 and R_2 are in parallel. Their effective resistance is

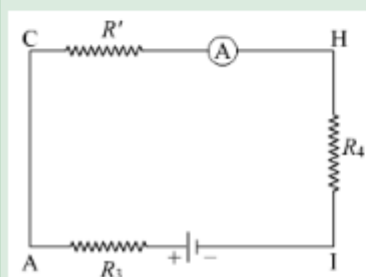
$$R' = \frac{R_1 \times R_2}{R_1 + R_2}$$



Now, R_3 , R' and R_4 are in series. Thus, the equivalent resistance of the circuit is

$$R_{eq} = \frac{R_1 \times R_2}{R_1 + R_2} + R_3 + R_4$$
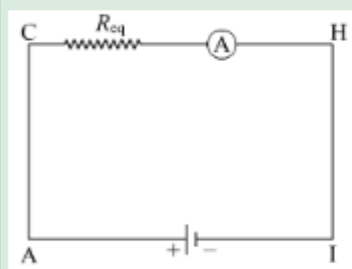
$$= \frac{R_1 R_2 + R_3 R_1 + R_3 R_2 + R_4 R_1 + R_4 R_2}{R_1 + R_2}$$



Hence, the current flowing in the circuit is

$$I = V/R_{eq} = \frac{V}{\frac{R_1 R_2 + R_3 R_1 + R_3 R_2 + R_4 R_1 + R_4 R_2}{R_1 + R_2}}$$

$$= \frac{V(R_1 + R_2)}{R_1 R_2 + R_3 R_1 + R_3 R_2 + R_4 R_1 + R_4 R_2}$$

where, V is the potential difference of the battery.

Question 8:

Three resistances x_1 , x_2 and x_3 are connected in a circuit in different ways. x is the effective resistance. The properties observed for these different ways of connecting x_1 , x_2 and x_3 are given below. Write the way in which they are connected in each case. (I-current, V potential difference, x-effective resistance)

1. Current I flows through x_1 , x_2 and x_3
2. x is larger than x_1 , x_2 and x_3
3. x is smaller than x_1 , x_2 and x_3
4. The potential difference across x_1 , x_2 and x_3 is the same
5. $x = x_1 + x_2 + x_3$
6. $x = \frac{1}{\frac{1}{x_1} + \frac{1}{x_2} + \frac{1}{x_3}}$

Answer

1. In this case, x_1 , x_2 and x_3 are connected in series.
2. In this case, x_1 , x_2 and x_3 are connected in series.
3. In this case, x_1 , x_2 and x_3 are connected in parallel.
4. In this case, x_1 , x_2 and x_3 are connected in parallel.
5. In this case, x_1 , x_2 and x_3 are connected in series.
6. In this case, x_1 , x_2 and x_3 are connected in parallel.

Question 9:

Solve the following problems.

1. The resistance of a 1 m long nichrome wire is 6 Ω . If we reduce the length of the wire to 70 cm. what will its resistance be?

Answer

Resistance of a wire is directly proportional to its length. Let R_1 and R_2 be the resistances of the nichrome wire at 100 cm (1 m) and 70 cm, respectively.

We know $R = \rho(L/A)$

$$\therefore R_1 = \rho (L_1/A) \dots\dots(i) \quad \text{and} \quad R_2 = \rho (L_2/A) \dots\dots(ii)$$

Dividing (ii) by (i), we get

$$R_2/R_1 = L_2/L_1 = 70/100$$

$$\Rightarrow R_2 = (70/100) \times R_1$$

$$\text{Now, } R_1 = 6 \, \Omega$$

$$\Rightarrow R_2 = (70/100) \times 6 = 0.7 \times 6$$

$$= 4.2 \, \Omega$$

Required Resistance = 4.2 Ω

2. When two resistors are connected in series, their effective resistance is $80\ \Omega$. When they are connected in parallel, their effective resistance is $20\ \Omega$. What are the values of the two resistances?

Answer

Let the two resistances be R_1 and R_2 . Therefore,

$$R_1 + R_2 = 80\ \Omega$$

$$\text{or, } R_1 = 80 - R_2 \quad \dots(i)$$

and

$$1/R_1 + 1/R_2 = 1/20$$

$$\Rightarrow R_1 R_2 = 20(R_1 + R_2)$$

$$\text{As, } R_1 = 80 - R_2$$

$$\Rightarrow (80 - R_2)R_2 = 20(80 - R_2 + R_2)$$

$$80R_2 - R_2^2 = 1600$$

$$R_2^2 - 80R_2 + 1600 = 0$$

$$(R_2 - 40)(R_2 - 40) = 0$$

$$\Rightarrow R_2 = 40\ \Omega$$

$$\text{From (i), we get } R_1 = 80 - 40 = 40\ \Omega$$

$$\mathbf{R_1 = 40\ \Omega \text{ and } R_2 = 40\ \Omega}$$

3. If a charge of $420\ \text{C}$ flows through a conducting wire in 5 minutes what is the value of the current?

Answer

Current flowing through the conducting wire is

$$I = \text{Charge}(Q) / \text{Time}(t)$$

$$\Rightarrow I = 420 / (5 \times 60) = 420 / 300 = 1.4\ \text{A}$$

Hence, the current flowing through the wire is $1.4\ \text{A}$.